

A voltage source $\underline{E} = 7 + \frac{14\sqrt{3}}{2}j[\dots 1.]$ powers a circuit, determining a current flow through this one of value $\underline{I} = 2e^{j\frac{\pi}{4}}[\dots 2.]$. Compute the complex power of this circuit, $\underline{S}$ 3, and explain the significance of the real part 4 and the imaginary part of this power 5, and state their measurements units 6. Find the sinusoidal expression of the voltage source $e(t)$ 7, and compute its value when $t=7[\text{ms}]$ 8 if the circuit works on the frequency $f=50[\dots 9.]$. One circuit element is a resistance. Compute its value starting from the active power 10. State the measurement units for the following quantities: $\bar{H}$ and ε 11 and 12.

Laural.Darabant@gmail.com

Ora: 14:25

Ora: 14:25

1. Volt, V

2. Ampere, A

$$3. \underline{S} = \underline{E} \cdot \underline{I}^* = (7 + \frac{14\sqrt{3}}{2}j) \cdot 2e^{-j\frac{\pi}{4}} = 14e^{j\frac{\pi}{3}} \cdot 2e^{-j\frac{\pi}{4}} = 28e^{j(\frac{\pi}{3} - \frac{\pi}{4})} = 28e^{j\frac{\pi}{12}} = 27,04 + 7,24j$$

4. P - active power

5. Q - reactive power

6. W (Watt) and VAr (Volt-Ampere reactive)

$$7. e(t) = 14\sqrt{2} \sin\left(\omega t + \frac{\pi}{3}\right)$$

$$8. e(7ms) = 14\sqrt{2} \sin\left(2\pi \cdot 50 \cdot 7 \cdot 10^{-3} + \frac{\pi}{3}\right) \cong 19,79 \sin(\pi \cdot 1,03) \cong [A]$$

9. Hz - Hertz

$$10. P = R \cdot I^2 = 27,04 \rightarrow R = \frac{P}{I^2} = \frac{27,04}{2^2} = \frac{27,04}{4} = 6,76[ohm]$$

11. A/m

12. 12. F/m