

We know the admittance  $\underline{Y} = \frac{1}{6} - \frac{1}{2\sqrt{3}}j$  [....1.]. This is obtained by connecting in parallel a resistance with ...2...The susceptance, representing the .....3....part of the admittance, can be computed with the formula.....4..... If the admittance is crossed by a current  $\underline{I} = 12e^{-j\pi}$  [5...], of frequency  $f=10$  [...6..], find the value of the voltage drop  $\underline{U}$  on this admittance 7. Write the sinusoidal expression of the voltage,  $u(t)$  8, and compute its value when  $t=1$  [ms] 9. Write the value 10 and the measurement 11 unit for the element connected in parallel with the resistance. State the measurement units for the following quantity:  $\mu_0$  12.

[Laural.Darabant@gmail.com](mailto:Laural.Darabant@gmail.com)

Ora: 16:26

1. Siemens, S – 0,8

2. a coil- 2

3. Imaginary - 2

4.  $B=1/\omega L$  2

5. A, Ampere -0,8

6. Hz (Hertz) -0,8

$$7. \underline{U} = \frac{\underline{I}}{\underline{Y}} = \frac{12e^{-j\pi}}{\frac{1}{6} - \frac{1}{2\sqrt{3}}j} = \frac{12e^{-j\pi}}{\frac{1}{3}e^{-j\frac{\pi}{3}}} = 36e^{j(-\pi+\frac{\pi}{3})} = 36e^{-j\frac{2\pi}{3}} [V] -3$$

$$8. u(t) = 36\sqrt{2}\sin\left(\omega t - \frac{2\pi}{3}\right) \text{ V}$$

$$9. u(1\text{ms}) = 36\sqrt{2}\sin\left(2\pi \cdot 10 \cdot 1 \cdot 10^{-3} + \frac{\pi}{4}\right) \cong \sin(\pi \cdot 0,45) \cong 8,35[V] - 3$$

$$10. \text{ and } 11. \frac{1}{\omega L} = B = \frac{1}{2\sqrt{3}} \rightarrow L = \frac{2\sqrt{3}}{\omega} = \frac{2\sqrt{3}}{2\pi \cdot 10} = 55,06[mH] \text{ 2 and 0,8}$$

12. H/m - 0,8